 


3-A

Netlist used

```
Q_3_a.spice
1  * CMOS Inverter VTC Simulation (VTC of inverter-1)
2  .include TSMC_180nm.txt
3  .param Wn = 18u
4  .param Wp = {2.5*Wn}
5  .param L = 0.18u
6  .global gnd
7  .subckt inverter in out vdd gnd Wn={Wn} Wp={Wp} L={L}
8  M1 out in gnd gnd CMOSN W={Wn} L={L}
9  M2 out in vdd vdd CMOSP W={Wp} L={L}
10 .ends inverter
11 Vdd vdd gnd 1.8
12 Vin in gnd 0
13 Xinv1 in vout1 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
14 Xinv2 vout1 vout2 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
15 .control
16 dc Vin 0 1.8 0.01
17 run
18 set curplottitle="mididoddisaipoojith-2025122010-3-A"
19 plot v(vout1) vs v(in)
20 .endc
21 .end
```

simulation data



VTC of inverter-1 (I1)

When a CMOS inverter drives another identical inverter, the input of the second inverter acts as a capacitive load on the first. Thus, the VTC of the first inverter remains essentially the same as a single CMOS inverter, with only a slight effect due to loading. The overall shape is unchanged.

3-B

Netlist used

simulation data

```

vil = 7.456705e-01
voh = 1.689961e+00
vih = 1.002331e+00
vol = 1.114904e-01
nmh = 6.876300e-01
nml = 6.341801e-01
ngspice 1 ->

```

```

Q3.bspice
1  * CMOS Inverter (to find the noise margin parameters)
2  .include TSMC_180nm.txt
3  .param Wn = 18u
4  .param Wp = {2.5*Wn}
5  .param L = 0.18u
6  .global gnd
7  .subckt inverter in out vdd gnd Wn={Wn} Wp={Wp} L={L}
8  M1 out in gnd gnd CMOSN W={Wn} L={L}
9  M2 out in vdd vdd CMOSP W={Wp} L={L}
10 .ends inverter
11 Vdd vdd gnd 1.8
12 Vin in gnd 0
13 Xinv1 in vout1 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
14 Xinv2 vout1 vout2 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
15 .control
16 dc Vin 0 1.8 0.002
17 run
18 let dV = deriv(v(vout1))
19 meas dc VIL find v(in) when dV=-1 cross=1
20 meas dc VOH find v(vout1) when dV=-1 cross=1
21 meas dc VIH find v(in) when dV=-1 cross=2
22 meas dc VOL find v(vout1) when dV=-1 cross=2
23 let NMH = VOH - VIH
24 let NML = VIL - VOL
25 print VIL VOH VIH VOL
26 print NMH NML
27 plot v(vout1) vs v(in)
28 .endc
29 .end

```

3-b) $V_{tn} = 0.54 \text{ V} = |V_{tp}|$

$V_{IL} = \frac{3V_{DD} + 5V_{tn} - 3|V_{tp}|}{8}$

$= \frac{3V_{DD} + 2V_{tn}}{8} = \frac{3(1.8) + 2(0.54)}{8}$

$V_{IL} = 0.81 \text{ V}$

$V_{OH} = \frac{7V_{DD} + V_{tn} + |V_{tp}|}{8}$

$V_{OH} = 1.71 \text{ V}$

$V_{IH} = \frac{5V_{DD} + 3V_{tn} - 5|V_{tp}|}{8}$

$V_{IH} = 0.99 \text{ V}$

$V_{OL} = \frac{V_{DD} - V_{tn} - |V_{tp}|}{8}$

$V_{OL} = 0.09 \text{ V}$

$NM_L = V_{IL} - V_{OL} = 0.72 \text{ V}$

$NM_H = V_{OH} - V_{IH} = 0.72 \text{ V}$

Reasons for Different Noise Margin Values

1) The formula we were using, derived by assuming no velocity saturation, no mobility degradation, no channel-length modulation, etc. In practical these effects will be there so we will get slightly different noise margin parameters.

3-C


Netlist used

simulation data

```

vil = 6.741419e-01
voh = 1.694980e+00
vih = 8.860775e-01
vol = 1.287589e-01
nmh = 8.089025e-01
nml = 5.453830e-01
ngspice 1 ->

```

 


```

Q3_c.spice
1  .include TSMC_180nm.txt
2  Vdd vdd 0 1.8
3  Vin in 0 0
4  M1000 vout in vdd vdd CMOSF w=50u l=2u
5  + ad=1.45n pd=0.158m as=1.3n ps=0.152m
6  M1002 voutf in 0 0 CMOSN w=25u l=2u
7  + ad=0.725n pd=0.108m as=0.975n ps=0.128m
8  M1001 voutf vout vdd vdd CMOSF w=50u l=2u
9  + ad=1.45n pd=0.158m as=1.3n ps=0.152m
10 M1003 voutf vout 0 0 CMOSN w=25u l=2u
11 + ad=0.725n pd=0.108m as=0.975n ps=0.128m
12 C1 vout vdd 0.30108f
13 C2 voutf vout 0.04038f
14 C4 vout vdd 0.00805f
15 C5 vout vdd 0.30108f
16 C7 voutf 0 0.96422f
17 C8 vdd 0 1.6689f
18 C9 vout 0 3.67844f
19 C10 vout 0 8.97733f
20 C11 vout 0 8.97733f
21 .dc Vin 0 1.8 0.002
22 .control
23 run
24 let dV = deriv(v(vout))
25 meas dc VIL find v(in) when dV=-1 cross=1
26 meas dc VOH find v(vout) when dV=-1 cross=1
27 meas dc VIH find v(in) when dV=-1 cross=2
28 meas dc VOL find v(vout) when dV=-1 cross=2
29 let NMH = VOH - VIH
30 let NML = VIL - VOL
31 print VIL VOH VIH VOL NMH NML
32 set curplottitle="mididoddaisaipoojith-2025122010-3-c"
33 plot v(vout) vs v(in)
34 endc

```

MAGIC layout

 

3-C	V _{IL}	V _{OH}	V _{IH}	V _{OL}	NM _H	NM _L
pre-layout	0.74	1.68	1.00	0.11	0.68	0.63 (V)
post-layout	0.67	1.69	0.88	0.12	0.80	0.54 (V)

↳ The difference b/w pre-layout and post-layout noise margins is due to parasitic capacitances and resistances extracted from layout. In post-layout case, these affect the VTC, which in turn alters V_{OH}, V_{OL}, V_{IL}, V_{IH}. So noise margin parameters change.

4-a) From 3-b $V_{TN} = |V_{TP}| = 0.54$
 $V_{OH} = 1.071 \text{ V}$ $V_{IL} = 0.81 \text{ V}$
 $V_{IH} = 0.99 \text{ V}$ $V_{OL} = 0.09 \text{ V}$

(9)
$$\frac{k_p \tau_{rise}}{C_L} = \frac{2[V_{OL} + |V_{TP}|]}{k_p(V_{DD} - V_{OL} - |V_{TP}|)^2} + \ln \left(\frac{V_{DD} + V_{OH} - 2V_{IL} + 2|V_{TP}|}{V_{DD} - V_{OL}} \right)$$

$$\Rightarrow \frac{k_p \tau_{rise}}{C_L} = \frac{2[0.81 + 0.54]}{(1.08 - 0.81 - 0.54)^2} + \ln \left(\frac{1.08 + 1.071 - 1.062 - 1.09}{1.08 - 1.071} \right)$$

$= 18.18$

$$\therefore \frac{k_p \tau_{rise}}{C_L} = 18.18$$

9i)
$$\frac{k_n \tau_{fall}}{C} = \frac{2(V_{DD} - V_{IH} + V_{TN})}{(V_{IH} - V_{TN})^2} + \ln \left(\frac{2(V_{IH} - V_{TN}) - V_{OL}}{V_{IH} - V_{TN}} \right)$$

$$\Rightarrow \frac{k_n \tau_{fall}}{C} = \frac{2(1.08 - 0.99 + 0.54)}{(0.99 - 0.54)^2} + \ln \left(\frac{2(0.99 - 0.54) - 0.09}{0.99 - 0.54} \right)$$

$= 18.21$

$$\therefore \frac{k_p \tau_{rise}}{C_L} = 18.18$$

$$\therefore \frac{k_n \tau_{fall}}{C} = 18.21$$

4-B


Netlist used

```

Q_4_b.spice
1  * F04 Inverter Chain Example (Measure Rise/Fall Times at C and D)
2  .include TSMC_180nm.txt
3  .param Wn=1.8u
4  .param Wp={2.5*Wn}
5  .param L=0.18u
6  .global gnd
7  .subckt inverter in out vdd gnd Wn={Wn} Wp={Wp} L={L}
8  M1 out in gnd gnd CMOSN W={Wn} L={L}
9  M2 out in vdd vdd CMOSP W={Wp} L={L}
10 .ends inverter
11 Vdd vdd gnd 1.8
12 Vin A gnd PWL(0n 0V 0.5n 1.8V 1.1n 1.8V 1.5n 0V 5n 0V)
13 Xin1 A B vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
14 Xin2 B C vdd gnd inverter Wn={4*Wn} Wp={4*Wp} L={L}
15 Xin3 C D vdd gnd inverter Wn={16*Wn} Wp={16*Wp} L={L}
16 Xin4 D E vdd gnd inverter Wn={64*Wn} Wp={64*Wp} L={L}
17 Xin5 E F vdd gnd inverter Wn={256*Wn} Wp={256*Wp} L={L}
18 Cload F gnd 1p
19 .control
20 tran 10p 5n
21 set curplottitle="mididoddisaipoojith-2025122010-4-B"
22 plot v(C) v(D)
23 meas tran trC TRIG v(C) VAL=0.18 RISE=1 TARG v(C) VAL=1.62 RISE=1
24 meas tran tfC TRIG v(C) VAL=1.62 FALL=1 TARG v(C) VAL=0.18 FALL=1
25 meas tran trD TRIG v(D) VAL=0.18 RISE=1 TARG v(D) VAL=1.62 RISE=1
26 meas tran tfD TRIG v(D) VAL=1.62 FALL=1 TARG v(D) VAL=0.18 FALL=1
27 print trC tfC trD tfD
28 .endc
29 .end

```

simulation data

 

```

trc = 1.615056e-10
tfc = 1.524097e-10
trd = 1.865704e-10
tfd = 1.671252e-10
ngspice 1 ->

```

The delays at node C and node D are not equal. The delay is proportional to the ratio $C(\text{ext})/C(\text{in})$. Since the effective external capacitance at node D is larger than that at node C, the delay observed at D is greater than the delay at C.

Netlist used

```

Q_4_c.spice
1  * F04 Inverter Chain (measure propagation delays for I3 and I4)
2  .include TSMC_180nm.txt
3  .param Wn=1.8u
4  .param Wp={2.5*Wn}
5  .param L=0.18u
6  .subckt inverter in out vdd gnd Wn={Wn} Wp={Wp} L={L}
7  M1 out in gnd gnd CMOSN W={Wn} L={L}
8  M2 out in vdd vdd CMOSP W={Wp} L={L}
9  .ends inverter
10 Vdd vdd 0 1.8
11 Vin A 0 PWL(0n 0V 0.5n 1.8V 1.1n 1.8V 1.5n 0V 5n 0V)
12 Xinv1 A B vdd 0 inverter Wn={Wn} Wp={Wp} L={L}
13 Xinv2 B C vdd 0 inverter Wn={4*Wn} Wp={4*Wp} L={L}
14 Xinv3 C D vdd 0 inverter Wn={16*Wn} Wp={16*Wp} L={L}
15 Xinv4 D E vdd 0 inverter Wn={64*Wn} Wp={64*Wp} L={L}
16 Xinv5 E F vdd 0 inverter Wn={256*Wn} Wp={256*Wp} L={L}
17 Cload F 0 1p
18 .control
19 tran 10p 5n
20 plot v(C) v(D)
21 meas tran tplh_i3 TRIG v(C) VAL=0.9 RISE=1 TARG v(D) VAL=0.9 RISE=1
22 meas tran tphl_i3 TRIG v(C) VAL=0.9 FALL=1 TARG v(D) VAL=0.9 FALL=1
23 meas tran tplh_i4 TRIG v(D) VAL=0.9 RISE=1 TARG v(E) VAL=0.9 RISE=1
24 meas tran tphl_i4 TRIG v(D) VAL=0.9 FALL=1 TARG v(E) VAL=0.9 FALL=1
25 let tpd_i3 =(tplh_i3 + tphl_i3)/2
26 let tpd_i4 =(tplh_i4 + tphl_i4)/2
27 print tpd_i3 tpd_i4
28 .endc
29 .end

```

simulation data

```

tpd_i3 = 1.045171e-10
tpd_i4 = 1.355980e-10
ngspice 1 ->

```

Inverter	t_{pd} (s)	t_{pd} (ns)
I3	1.045171×10^{-10}	0.105 ns
I4	1.355980×10^{-10}	0.136 ns


The propagation delays of inverters I3 and I4 are not the same. Inverter I3 shows a smaller delay compared to I4 because I3 is closer to the driving node and experiences less effective loading, while I4 sees additional capacitive loading and propagation through more stages. Since delay is proportional to the external load capacitance, the larger loading at node D4 increases its delay. Hence, $tpd(I4)$ is greater than $tpd(I3)$.

4-D

Netlist used

```
Q_4_d.spice
1  *CMOS Inverter Chain (IDD)
2  .include TSMC_180nm.txt
3  .param Wn=1.8u
4  .param Wp={2.5*Wn}
5  .param L=0.18u
6  .subckt inverter in out vdd vss Wn={Wn} Wp={Wp} L={L}
7  M1 out in vss vss CMOSN W={Wn} L={L}
8  M2 out in vdd vdd CMOSP W={Wp} L={L}
9  .ends inverter
10 Vdd vdd 0 1.8
11 Vin A 0 PWL(0n 0V 0.5n 1.8V 1.1n 1.8V 1.5n 0V 5n 0V)
12 Xin1 A B vdd 0 inverter Wn={Wn} Wp={Wp} L={L}
13 Xin2 B C vdd 0 inverter Wn={4*Wn} Wp={4*Wp} L={L}
14 VDD3 vdd3 0 1.8
15 VSS3 gnd3 0 0
16 Xin3 C D vdd3 gnd3 inverter Wn={16*Wn} Wp={16*Wp} L={L}
17 Xin4 D E vdd 0 inverter Wn={64*Wn} Wp={64*Wp} L={L}
18 Xin5 E F vdd 0 inverter Wn={256*Wn} Wp={256*Wp} L={L}
19 Cload F 0 1p
20 .control
21 tran 10p 5n
22 set curplottitle="mididoddisaipoojith-2025122010-4-D"
23 plot -I(VDD3)
24 .endc
25 .end
```

simulation data

 

The supply current waveform of inverter I3 represents the dynamic current drawn from the source during switching. When the input switches, both the NMOS and PMOS conduct simultaneously for a short duration, creating a direct path from VDD to gnd. These effects result in a sharp positive current spike. Once the output reaches a stable logic level, the conduction path is cut off and the supply current drops back close to zero. A small negative dip is also observed in the waveform, which occurs because during certain transitions a portion of the charge stored in the output or parasitic capacitances flows back into the supply rail through the PMOS device.

4-E


Netlist used

```

Q_4_e.spice
1  *CMOS Inverter Chain (ISS)
2  .include TSMC_180nm.txt
3  .param Wn=1.8u
4  .param Wp={2.5*Wn}
5  .param L=0.18u
6  .subckt inverter in out vdd vss Wn={Wn} Wp={Wp} L={L}
7  M1 out in vss vss CMOSN W={Wn} L={L}
8  M2 out in vdd vdd CMOSP W={Wp} L={L}
9  .ends inverter
10 Vdd vdd 0 1.8
11 Vin A 0 PWL(0n 0V 0.5n 1.8V 1.1n 1.8V 1.5n 0V 5n 0V)
12 Xinv1 A B vdd 0 inverter Wn={Wn} Wp={Wp} L={L}
13 Xinv2 B C vdd 0 inverter Wn={4*Wn} Wp={4*Wp} L={L}
14 VDD3 vdd3 0 1.8
15 VSS3 gnd3 0 0
16 Xinv3 C D vdd3 gnd3 inverter Wn={16*Wn} Wp={16*Wp} L={L}
17 Xinv4 D E vdd 0 inverter Wn={64*Wn} Wp={64*Wp} L={L}
18 Xinv5 E F vdd 0 inverter Wn={256*Wn} Wp={256*Wp} L={L}
19 Cload F 0 1p
20 .control
21 tran 10p 5n
22 set curplottitle="mididoddisaipoojith-2025122010-4-E"
23 plot -I(VSS3)
24 .endc
25 .end

```

simulation data

 


The ground current waveform of inverter I3 represents the transient current flowing into the ground during switching. When the input changes, the NMOS device conducts strongly, discharging the output node to ground and creating a sharp negative current spike (negative because current is defined entering the ground node). Once the output stabilizes, the direct discharge path is cut off and the current returns close to zero. A small positive bump is also seen, which arises from charge redistribution in the output and parasitic capacitances, where some stored charge flows back from the ground node.


```

Q 5.spice
1  .include TSMC_180nm.txt
2  .param Wn=1.8u
3  .param Wp={2.5*Wn}
4  .param L=0.18u
5  .subckt inverter in out vdd gnd Wn={Wn} Wp={Wp} L={L}
6  M1 out in gnd gnd CMOSN W={Wn} L={L}
7  M2 out in vdd vdd CMOSP W={Wp} L={L}
8  .ends inverter
9  Vdd vdd 0 1.8
10 Vin A 0 PWL(0n 0V 0.5n 1.8V 1.1n 1.8V 1.5n 0V 5n 0V)
11 Xin1 A B vdd 0 inverter Wn={Wn} Wp={Wp} L={L}
12 .param scale=1
13 Xin2 B C vdd 0 inverter Wn={scale*Wn} Wp={scale*Wp} L={L}
14 .control
15 tran 10p 5n
16 meas tran tplh TRIG v(A) VAL=0.9 RISE=1 TARG v(B) VAL=0.9 RISE=1
17 meas tran tphl TRIG v(A) VAL=0.9 FALL=1 TARG v(B) VAL=0.9 FALL=1
18 let tpd =(tplh + tphl)/2
19 print tpd
20 .endc
21 .end

```

simulation data

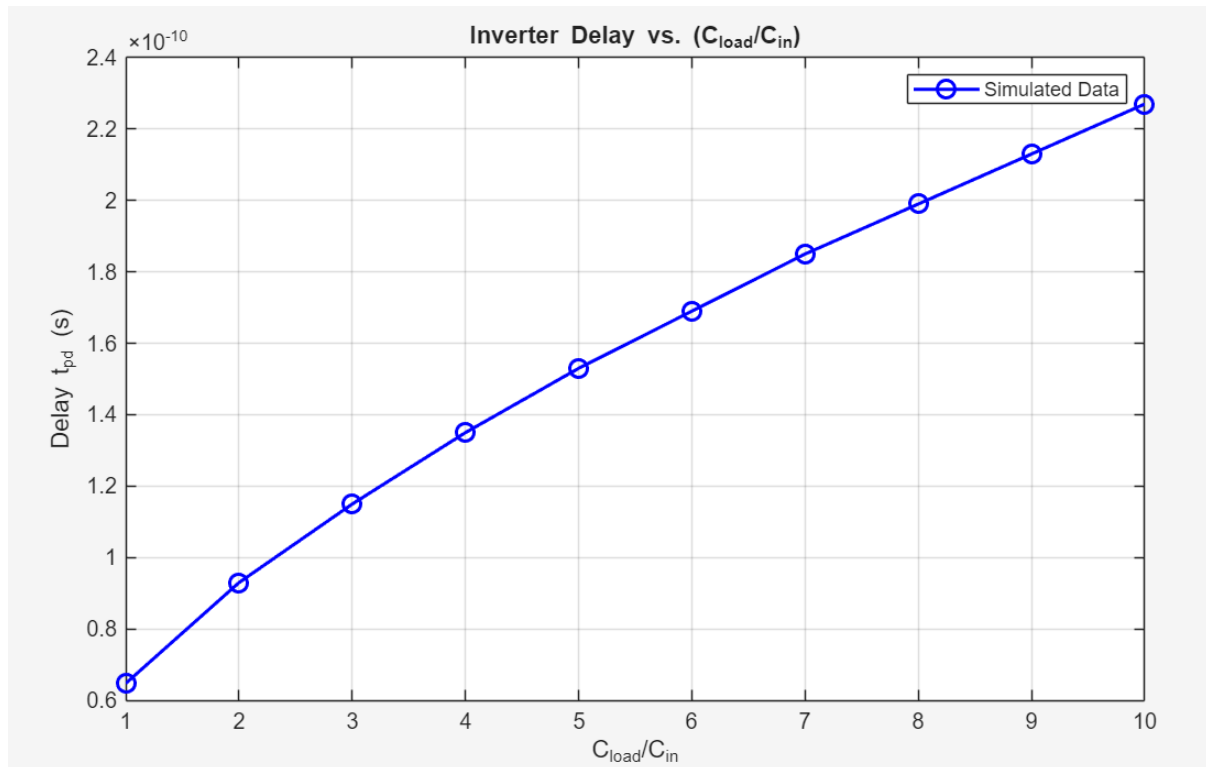

Delay unit = $1.75e-11$ s per unit C_{load}/C_{in}
 absolute Parasitic delay = $5.92e-11$ s

For delay characterization, the test circuit consists of two cascaded CMOS inverters. The first inverter acts as the device under test, and its output delay is measured with respect to its input. The second inverter is connected as a load, and its transistor widths are scaled to vary the effective load capacitance C_{load} , presented to the first inverter. Since the input capacitance of the first inverter, C_{in} , is fixed, the ratio C_{load}/C_{in} can be controlled by adjusting the scaling factor of the second inverter. A pulse input is applied to the first inverter to find the propagation delay. t_{pd} is then obtained for each load condition. By plotting t_{pd} versus C_{load}/C_{in} , the delay is verified to follow the logical effort form $t_{pd}=p+g.(C_{load}/C_{in})$, where the intercept p represents the absolute parasitic delay of the inverter and the slope g corresponds to the delay unit.

6-A

Netlist used

```

1 .include TSMC_180nm.txt
2 .param Wn = 10u
3 .param Wp = 25u
4 .param L = 2u
5 .param VDD = 1.8
6 .global gnd
7 .subckt inverter in out vdd gnd Wn={Wn} Wp={Wp} L={L}
8 M1 out in gnd gnd CMOSN W={Wn} L={L}
9 M2 out in vdd vdd CMOSP W={Wp} L={L}
10 .ends inverter
11 Vdd vdd gnd {VDD}
12 X1 n1 n2 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
13 X2 n2 n3 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
14 X3 n3 n4 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
15 X4 n4 n5 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
16 X5 n5 n6 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
17 X6 n6 n7 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
18 X7 n7 n8 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
19 X8 n8 n9 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
20 X9 n9 n10 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
21 X10 n10 n11 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
22 X11 n11 n12 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
23 X12 n12 n13 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
24 X13 n13 n14 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
25 X14 n14 n15 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
26 X15 n15 n16 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
27 X16 n16 n17 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
28 X17 n17 n18 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
29 X18 n18 n19 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
30 X19 n19 n20 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
31 X20 n20 n21 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
32 X21 n21 n22 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
33 X22 n22 n23 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
34 X23 n23 n24 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
35 X24 n24 n25 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
36 X25 n25 n26 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
37 X26 n26 n27 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
38 X27 n27 n28 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
39 X28 n28 n29 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
40 X29 n29 n30 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
41 X30 n30 n31 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
42 X31 n31 n1 vdd gnd inverter Wn={Wn} Wp={Wp} L={L}
43 .ic V(n1)=0.1
44 .control
45 tran 0.1n 0.4u
46 set curplottitle="mididoddaisaipoojith-2025122010-6-A"
47 plot v(n1)
48 meas tran Tperiod TRIG v(n1) VAL=0.9 RISE=2 TARG v(n1) VAL=0.9 RISE=
49 @eas tran tpdHL TRIG v(n1) VAL=0.9 FALL=3 TARG v(n2) VAL=0.9 FALL=3
50 meas tran tpdLH TRIG v(n1) VAL=0.9 RISE=3 TARG v(n2) VAL=0.9 RISE=3
51 let Davg =((tpdHL+tpdLH)/2)
52 print Tperiod
53 print Davg
54 .endc
55 .end
56


```

simulation data

```

fro = 9.732265e+06
delay = 1.657195e-09
ngspice 1 ->



```

 

From the NGSPICE simulation, the delay obtained directly from inverter propagation delay measurement is approximately equal to $T/62$, where T is the oscillation period of the 31-stage ring oscillator. This confirms the theoretical relation $f_{RO}=1/(62D)$

6-B

MAGIC layout

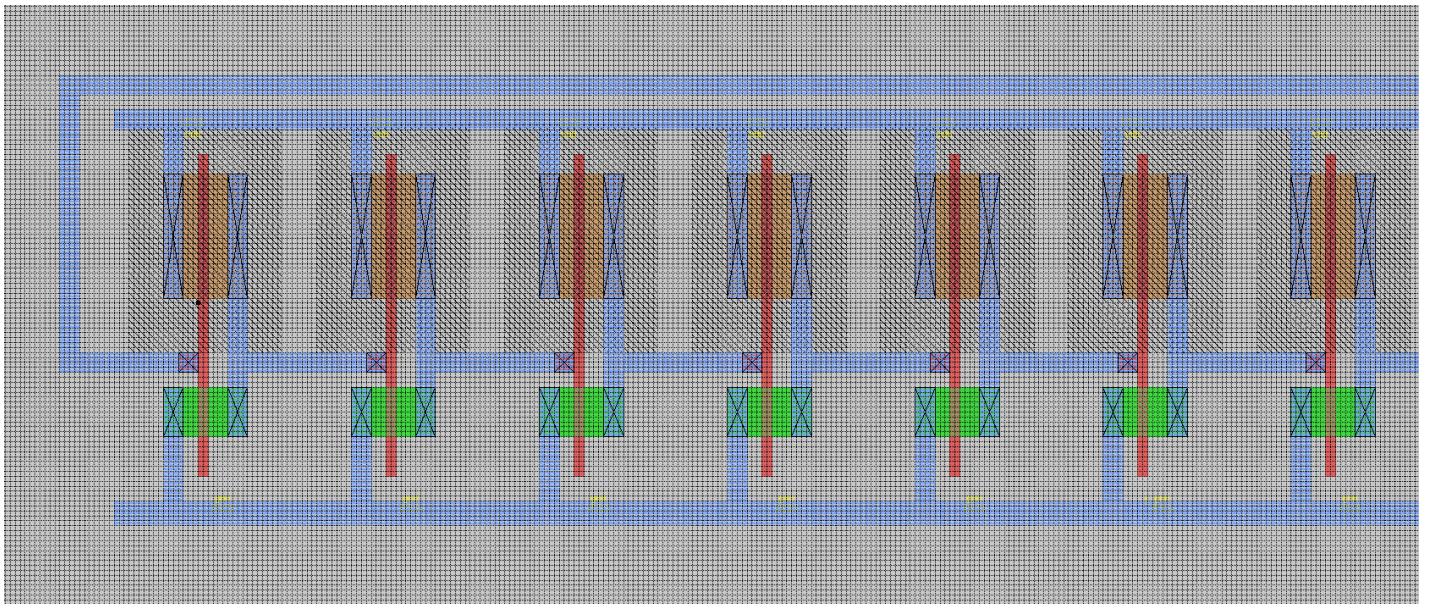 


6-C

Extracted from magic

simulation data

```
Ubuntu-24.04 > home > poojith > magic > inv_final.spice
1  * SPICE3 file created from inv_final.ext - technology: scmos
2
3  .option scale=90n
4
5  M1000 a_458_n27# a_420_n27# vdd w_442_n10# pfet w=25 l=2
6  + ad=0.2n pd=66u as=0.175n ps=64u
7  M1001 a_306_n27# a_268_n27# gnd Gnd nfet w=10 l=2
8  + ad=80p pd=36u as=70p ps=34u
9  M1002 a_686_n27# a_648_n27# gnd Gnd nfet w=10 l=2
10 + ad=80p pd=36u as=70p ps=34u
11 M1003 a_344_n27# a_306_n27# vdd w_328_n10# pfet w=25 l=2
12 + ad=0.2n pd=66u as=0.175n ps=64u
13 M1004 a_838_n27# a_800_n27# gnd Gnd nfet w=10 l=2
14 + ad=80p pd=36u as=70p ps=34u
15 M1005 a_230_n27# a_192_n27# vdd w_214_n10# pfet w=25 l=2
16 + ad=0.2n pd=66u as=0.175n ps=64u
17 M1006 a_268_n27# a_230_n27# gnd Gnd nfet w=10 l=2
18 + ad=80p pd=36u as=70p ps=34u
19 M1007 a_990_n27# a_952_n27# vdd w_974_n10# pfet w=25 l=2
20 + ad=0.2n pd=66u as=0.175n ps=64u
21 M1008 a_420_n27# a_382_n27# gnd Gnd nfet w=10 l=2
22 + ad=80p pd=36u as=70p ps=34u
23 M1009 a_40_n27# a_2_n27# vdd w_24_n10# pfet w=25 l=2
24 + ad=0.2n pd=66u as=0.175n ps=64u
25 M1010 a_192_n27# a_154_n27# vdd w_176_n10# pfet w=25 l=2
26 + ad=0.2n pd=66u as=0.175n ps=64u
27 M1011 a_116_n27# a_78_n27# vdd w_100_n10# pfet w=25 l=2
28 + ad=0.2n pd=66u as=0.175n ps=64u
29 M1012 a_40_n27# a_2_n27# gnd Gnd nfet w=10 l=2
30 + ad=80p pd=36u as=70p ps=34u
31 M1013 a_800_n27# a_762_n27# gnd Gnd nfet w=10 l=2
32 + ad=80p pd=36u as=70p ps=34u
33 M1014 a_952_n27# a_914_n27# gnd Gnd nfet w=10 l=2
34 + ad=80p pd=36u as=70p ps=34u
```
 
```
fro = 6.202829e+06
delay = 2.600270e-09
ngspice 1 ->
```



pre-layout simulation results

```
fro = 9.732265e+06  
delay = 1.657195e-09  
ngspice 1 ->
```

post-layout simulation results

```
fro = 6.202829e+06  
delay = 2.600270e-09  
ngspice 1 ->
```

The post-layout simulation shows a difference compared to the pre-layout case. The delay of each inverter stage increases after layout due to the additional parasitic capacitances and resistances introduced by interconnects. As a result, the overall oscillation frequency of the ring oscillator decreases compared to the ideal schematic-based prediction.